Electricity Transfer — Investigation

Chapter 4 · Energy Transfer · Week 5 (Day 2)

Name: _____ Date: _____

BIG QUESTION

What evidence shows that electric current can transfer energy from place to place?

PREDICT

What will the device do when the circuit is complete?

SAFETY

Low-voltage battery only (AA/AAA/D cell). No wall outlets. No coin cells.

MODEL

Fill in the model for your circuit:

BATTERY	CIRCUIT	DEVICE	CHANGE

The device can light up (bulb/LED), make sound (buzzer), or move (motor).

OBSERVE

1. Complete the circuit. What changed in the device?

2. Break the circuit (disconnect one wire). What stops?

CLASSIFY

Did the energy only MOVE, only CHANGE FORM, or BOTH? Circle one and explain.

TRANSFER **TRANSFORMATION** **BOTH**

EXPLAIN

What evidence shows that electric current transferred energy from the battery to the device?